

Digital Design : Tutorial


1. Minimise the following using Karnaugh maps

a. $F(a,b,c) = \sum m(0,1,3,4,6)$

b. $F(a,b,c,d) = \sum m(2,3,7,9, 11,12,15)$

c. $F(a,b,c,d,e) = \sum m(5,6,7,9,11,17,19,21,25,26,27,30,31)$

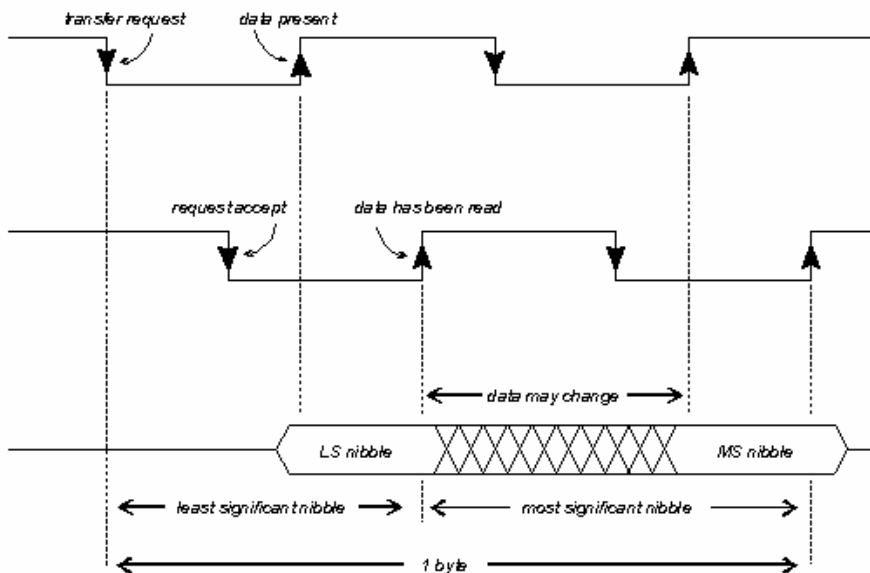2. Describe the different graphical aspects of this waveform diagram. Ignore the purpose of the diagram.




3. Convert the following 4 variable function to a standard Karnaugh map.


$$F(a,b,c,d) = \sum m(1,2,4,5,7,9,11,12,13,15)$$

Convert this 4 variable Karnaugh map to a 3 variable map entered Karnaugh map with **d** as the map entered variable.

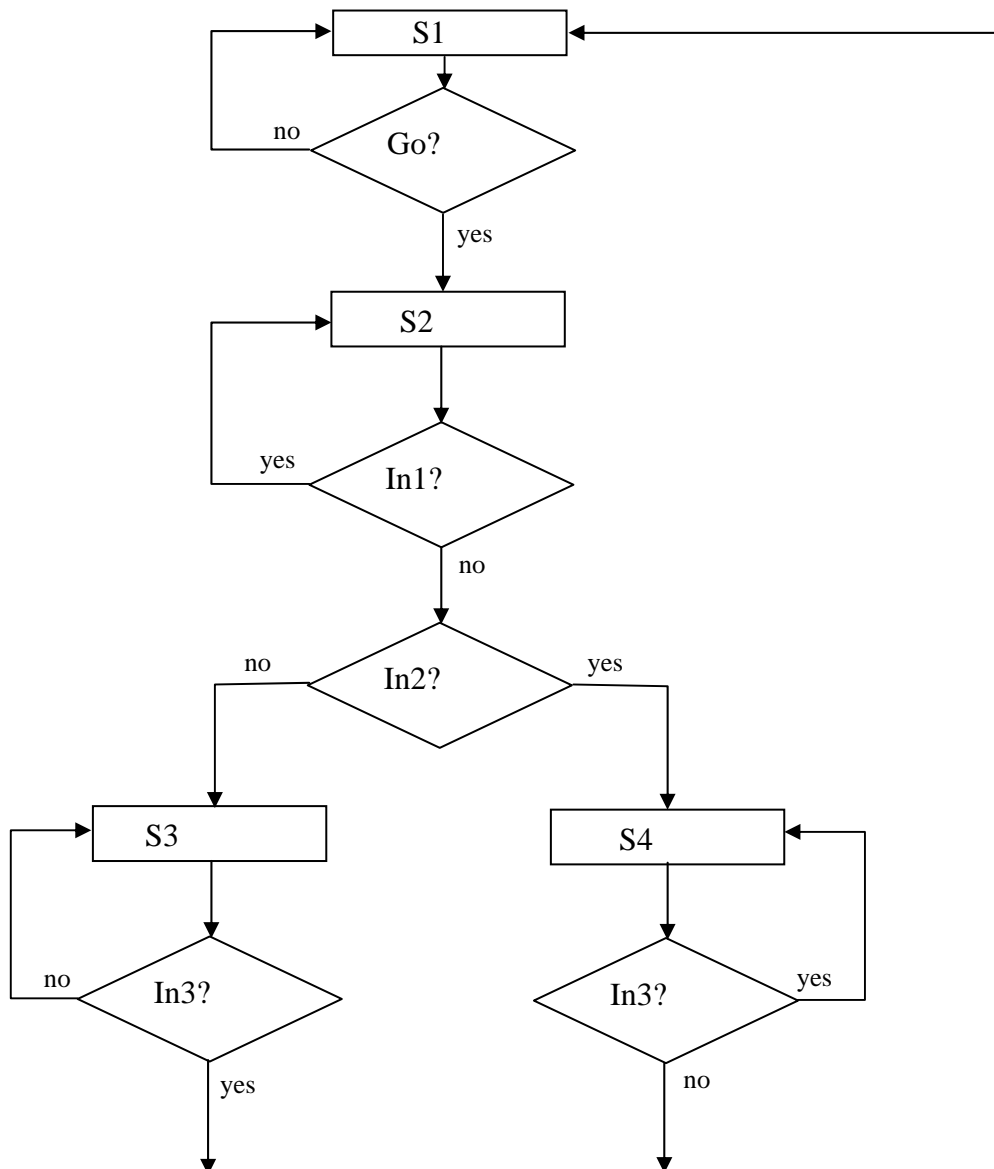
4. Answer the following questions
- Show how a glitch pulse can be created by a race condition setup by a single input signal.
 - Describe the operation of a D-type flip-flop.
 - Draw the structure of a Moore state machine.
 - Outline the problem of state consistency.
 - State the “asynchronous rule” for state assignment and indicate why it is important when dealing with asynchronous input signals.
5. What are the rules to produce a mapping from a Variable Entered Karnaugh Map (VEM).
6. Convert the following ASM chart to a state diagram. There are 4 states and 4 input signals



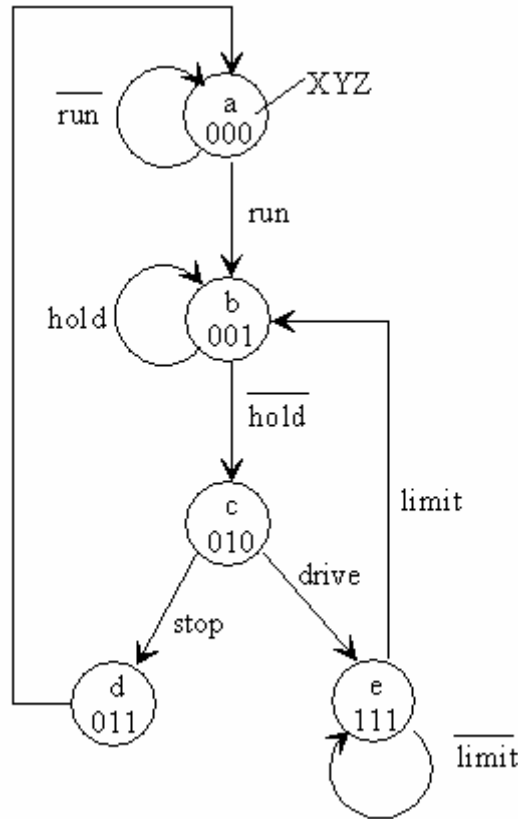7. Convert the state diagram of question 6 to a set of excitation equations for a D-type implementation of the state machine.
8. Convert the following state diagram to a set of D-type excitation equations.




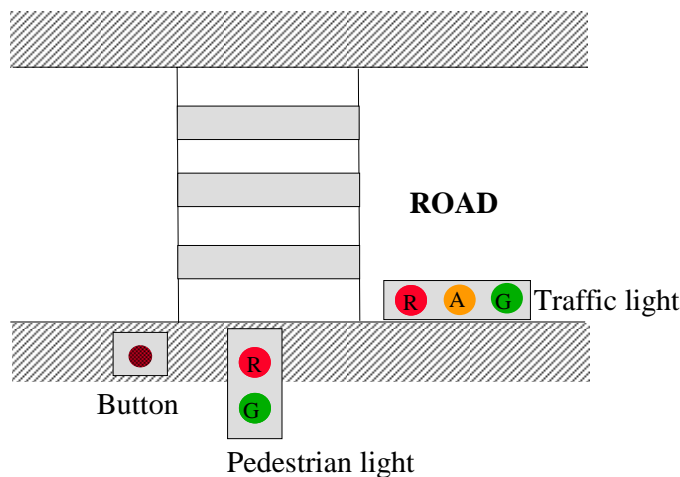9. Design a state machine to control a simple. “pedestrian crossing”.



10. Design a state machine to detect the value ‘10101’ in a serial stream of data.

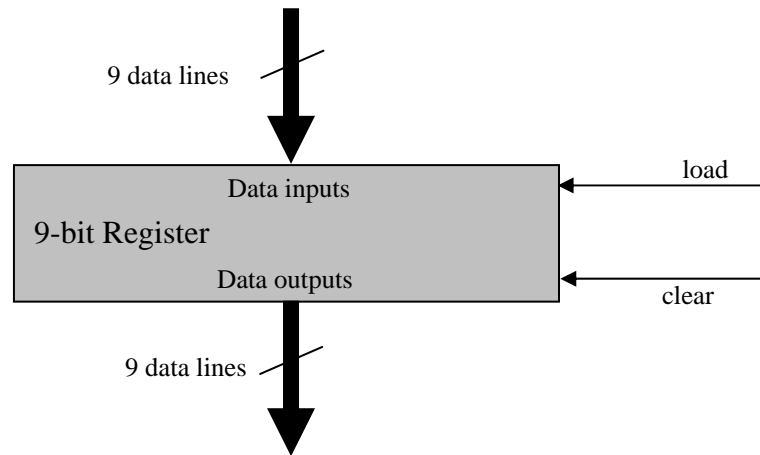11. List the steps required to solve a state machine problem that starts with a specification and finishes with a D-type flip-flop implementation.
12. List a general set of data components that can be used for digital system design.
13. Design a state machine based system to count the number of '1's in a register of length 9 bits. The starting point for your design is as follows



There are two control inputs – load and clear

14. (Exam question from 2003)

A manufacturer of vacuum cleaners wishes to experiment with robotic cleaners. They plan to design a cheap model that has little intelligence that bumps its way around a room in an almost random manner. It is proposed to build a series of test versions to evaluate the concept.

This initial version has the following hardware features

- A start button
- Motors can drive forward, backwards, turn left, turn right, and stop
- Three bump sensors, front left, front right, and rear provide detection of the environment
- An on-board timer, when triggered, gives a signal after 2 seconds

The operational requirements are

- On start drive forward.
- If left bump activated, turn right for 2 seconds then drive forward.
- If right bump activated, turn left for 2 seconds then drive forward.
- If both left and right bump activated, reverse for 4 seconds, turn right for 2 seconds, then drive forward.
- If rear bump, drive forward for 2 seconds, turn left for 2 seconds, then drive forward.

The control system is to be built as a state diagram.

- Draw a system block diagram showing the various subsystems and the relevant signals.
- Create a state diagram for the vehicle controller.
- From the state diagram derive a set of excitation equations for a D-type flip-flop implementation.
- Suggest changes to the hardware and state diagram to allow the following modification
 - If both left and right bump activated, reverse for 2 seconds, increment a 3-bit counter.
 - If counter is less than 4 turn right for 2 seconds, then drive forward
 - If counter is greater than 4 turn left for 2 seconds, then drive forward
(note : when counter is at 7 the next count sets count to zero)

